




Faculty of Science

Department of Physics

Laboratory Report Cover Page

Course Number	ELE404
Course Title	Electronic Circuits I
Semester/Year	04/2024
Instructor	Surinder Jassar
TA Name	Hanieh Ashrafirad
Section Number	6
Report Title	Design Project

Student Name	Student ID	Signature
Maryam Ramzaan	89038	

(Note: remove the first 4 digits from your student ID)

**By signing above you attest that you have contributed to this submission and confirm that all work you have contributed to this submission is your own work. Any suspicion of copying or plagiarism in this work will result in an investigation of Academic Misconduct and may result in a "0" on the work, an "F" in the course, or possibly more severe penalties, as well as a Disciplinary Notice on your academic record under the Student Code of Academic Conduct, which can be found online at: <http://www.rverson.ca/content/dam/senate/policies/pol60.pdf>*

Table of Contents

1. Introduction	R2
2. Objectives	R2
3. Circuit under Test	R2
4. Justifications	R4
5. Conclusions and Remarks	R5
6. Appendix: Handwritten Calculations	R9

Introduction

This is a design project focused on creating a transistor amplifier that is multistage and inverting. The results of this lab will aid in analyzing and testing this amplifier. This will be accomplished through the software MultiSim.

Objectives

Build an amplifier with the listed requirements

- Power supply: +10 V relative to the ground;
- Quiescent current drawn from the power supply: no larger than 10 mA;
- No-load voltage gain (at 1 kHz): $|A_{vo}| = 50 (\pm 10\%)$;
- Maximum no-load output voltage swing (at 1 kHz): no smaller than 8 V peak to peak;
- Loaded voltage gain (at 1 kHz and with $R_L = 1\text{ k}\Omega$): no smaller than 90% of the no-load voltage gain;
- Maximum loaded output voltage swing (at 1 kHz and $R_L = 1\text{ k}\Omega$): no smaller than 4 V peak to peak;
- Input resistance (at 1 kHz): no smaller than 20 k Ω ;
- Amplifier type: inverting or non-inverting;
- Frequency response: 20 Hz to 50 kHz (–3dB response);
- Type of transistors: BJT;
- Number of transistors (stages): no more than 3;
- Resistances permitted: values smaller than 220 k Ω from the E24 series;
- Capacitors permitted: 0.1 μF , 1.0 μF , 2.2 μF , 4.7 μF , 10 μF , 47 μF , 100 μF , 220 μF ;
- Other components (BJTs, diodes, Zener diodes, etc.): only from your ELE404 lab kit.

Circuit Under Test

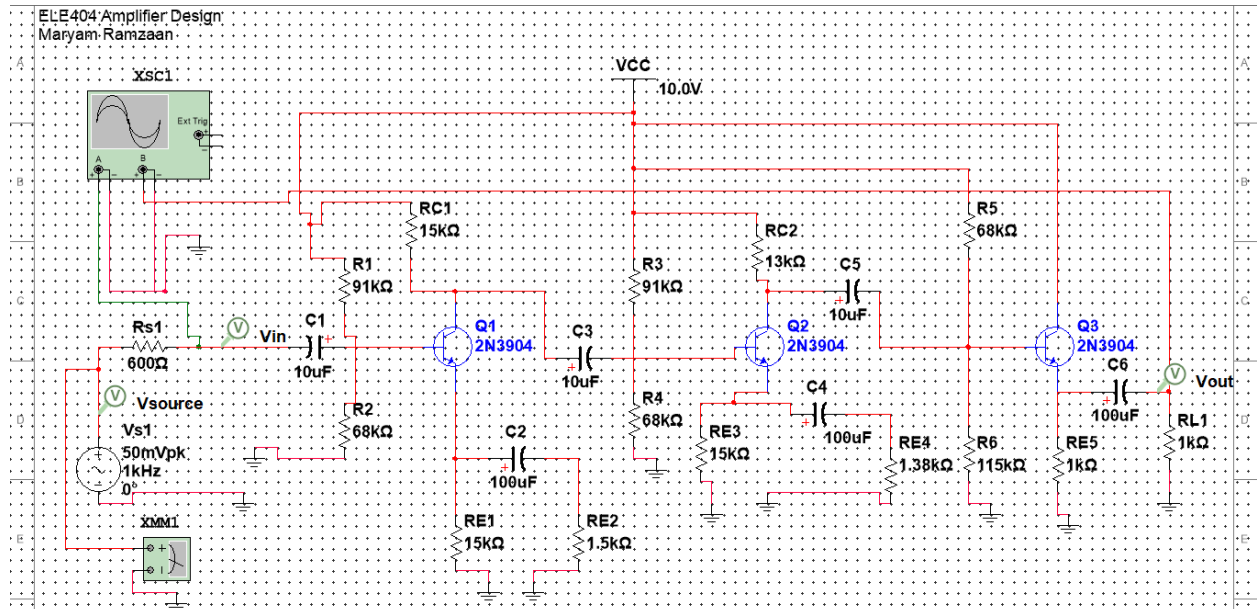


Figure 1: Amplifier circuit simulation created by cascading two CE amplifiers with a CC amplifier

Graphs

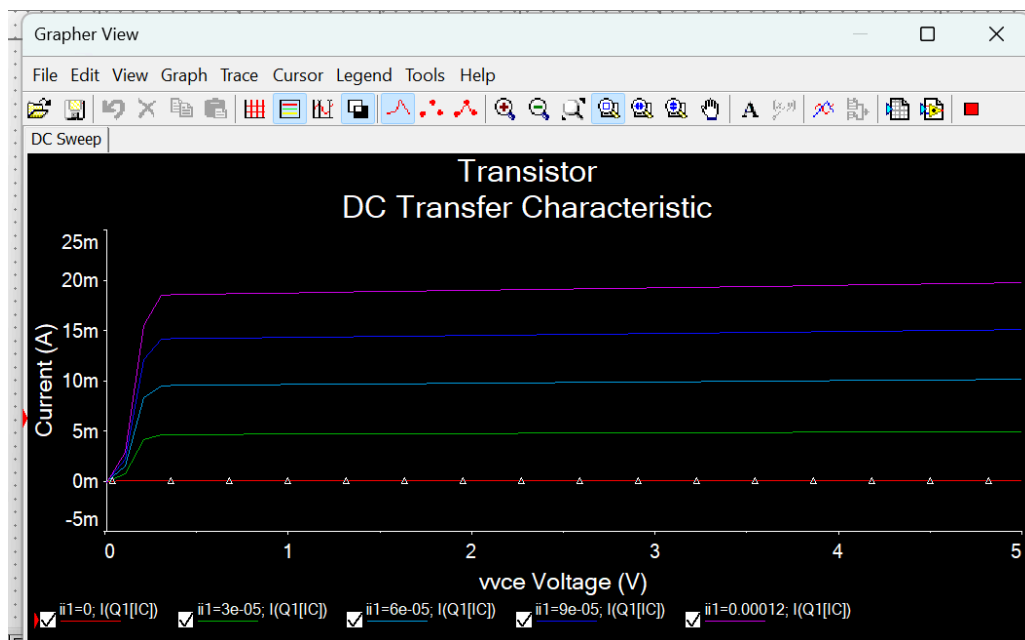


Figure 2: characteristic graph of the 2N3904 BJT

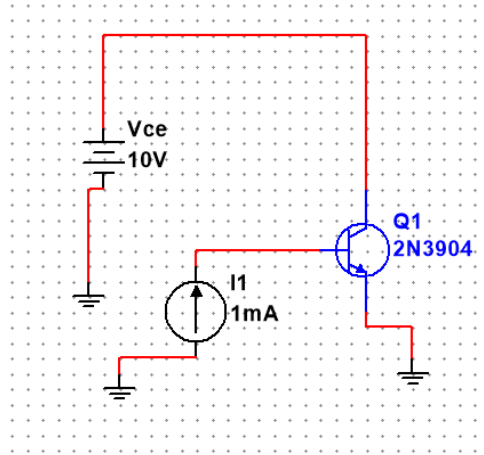


Figure 1b: The circuit used to create Figure 1a.

Justifications

Calculation Process

To design an amplifier that meets the stated objectives, it was assumed that a circuit with two common emitter BJTs and a common collector would be suitable. A voltage source of 50mVpk with a frequency of 1kHz was used to power the circuit, as well as a Vcc value of 10V. Three NPN Bipolar junction transistors were used as well as six capacitors to separate each of the three transistors followed by a load resistor R_L which was removed at certain points of this project to determine whether its presence would create changes among other measurements in the circuit. Furthermore, the chosen load line was 5V for the operation point, and 4.25 for the corresponding CE Voltage for this project although it is not shown and done manually.

As for the calculations, the voltage gain was considered first to fulfill the requirement for $A_{vo} \leq 50$. Since $A_{vo} = A_{vo1} \times A_{vo2} \times A_{vo3}$, and since the third amplifier is a common collector one, its $A_{vo} = 1$ because voltage gains of the CC amplifier are close to unity, and since the rest of the BJTs were CE, it made sense to assume $A_{vo1} = A_{vo2}$. Two numbers with a product of 50 is about $\sqrt{50} = \pm 7.1$. Throughout the calculation, it was recognized that both no-voltage gains needed to be -7.1, and that would yield a non-inverting amplifier as the product would be a positive A_{vo} of $50 \frac{V}{V}$. Apart from making calculations simpler, the CC amplifier would not be impacted by the removal and addition of the load resistor, making the circuit stable.

To determine the values of R_{ES} and R_6 , the third amplifier, or stage 3 was considered. Since the values of the resistors could only be those found in the ELE404 lab kit, it was assumed that R_5

had a value of $68k\Omega$. To find R_{E3} , the second stage was considered, and Kirchoffs voltage law and R_{c2} and R_{E4} at the transistor, Q2. Lastly, the capacitor values were calculated for best and worst cases, as well as the quiescent current. All capacitors that were positioned before the BJT, was given the value of $10\mu F$, and the capacitors parallel to the R_e in each of the three stages were $100\mu F$.

Experimental Results

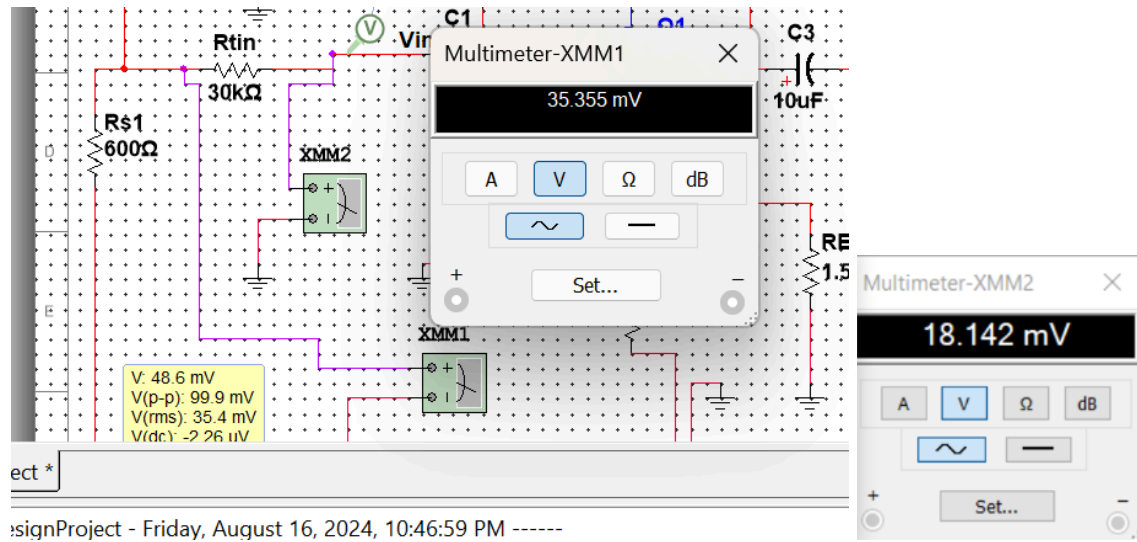


Figure : the multimeter placed before the R_{tin} resistor provides the V_t value while the one after provides the V_i

Using the information from Figure above, a new R_{tin} can be calculated with the following formula:

$$R_i = R_{t,in} \left(\frac{v_i}{v_t - v_i} \right)$$

$R_{i1,calculated}$ [k Ω]	R_{in} [k Ω]	V_t [V]	V_i [V]	$R_{i1,measured}$ [k Ω]
38.96	30	35.02	18.14	32.251

The percentage error between the calculated and the measured input resistance is as follows:

$$\begin{aligned}
 e\% &= \frac{\text{calculated value} - \text{measured value}}{\text{measured valued}} \times 100 \\
 &= \frac{38.96 - 32.251}{32.251} \times 100
 \end{aligned}$$

$$e\% = 20.8\%$$

The percentage error is about 20% and this could be the result of managing significant digits in calculations or general miscalculations. However, the percentage is well under 50% so it is acceptable and valid for this experiment.

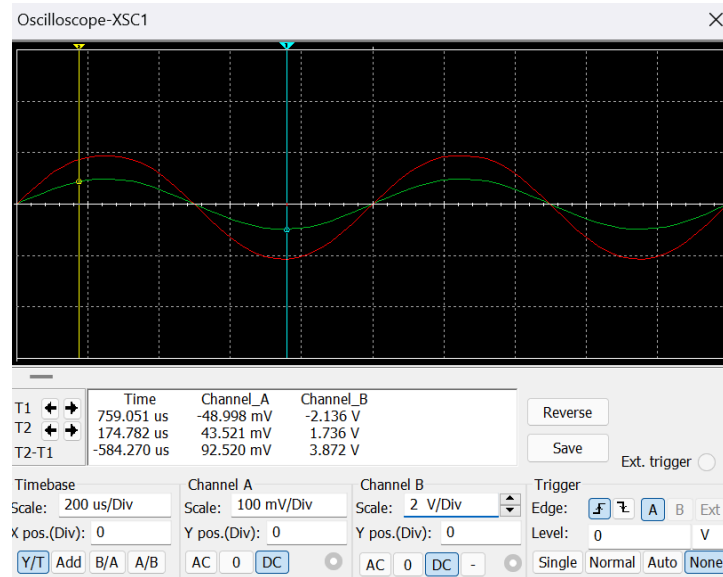


Figure 1a: input and output graph for $R_L = 1k\Omega$

$V_{I,PP}$ [mV]	$V_{O,PP}$ [mV]
92.520	3.872

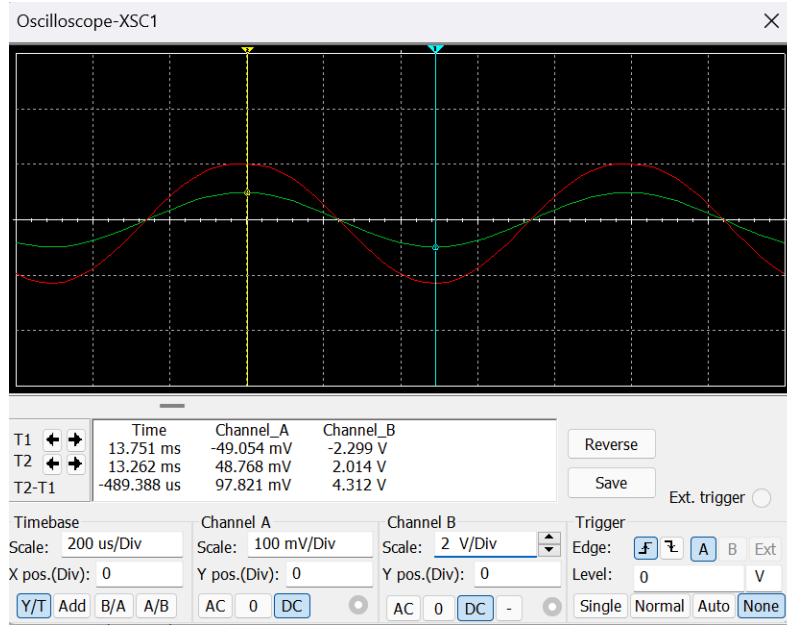


Figure 1b: input and output graph for $R_L = \infty$

$V_{I,PP}$ [mV]	$V_{O,PP}$ [V]
97.821	4.312

Conclusion

According to the results of the project, the majority of the requirements were met. If I could improve this experiment, I would need to make some changes in my choice of amplifiers and the resistors to ensure that there was voltage swing of 8V, and perhaps try different methods of calculations to increase the precision of my calculations to the results percentage.